

ARUS BOLAK-BALIK

Osiloskop = mengukur tegangan max

$$E = E_{\max} \cdot \sin \omega.t$$

E_{efektif} = yang diukur oleh voltmeter

E_{\max} = yang belum terukur

E_{pp} = dari puncak ke puncak

ω = frekwensi anguler

t = waktu

V_{\max} = tegangan maksimum

I_{\max} = Arus maksimum



T = periode

$$E_{\text{efektif}} = \frac{V_{\max}}{\sqrt{2}}$$

$$I_{\text{efektif}} = \frac{i_{\max}}{\sqrt{2}} \quad \rightarrow \quad I_{\text{efektif}} = I_{\max} \left\{ \sqrt{\frac{1}{T} \int_0^T \sin^2 \left(\frac{2\pi}{T} t \right) dt} \right\}$$

$$E_{\text{pp}} = 2 \cdot E_{\max}$$




I. Resistor pada DC-AC

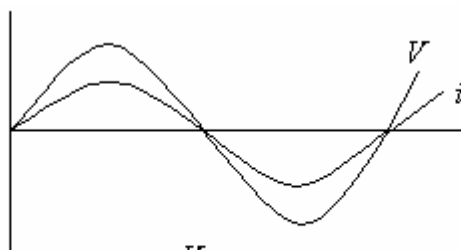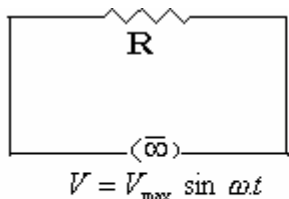

$$i = \frac{V}{R} = i_{\max} \sin \omega t$$

$$V = i \cdot R$$

II. Induktor (L) pada DC-AC

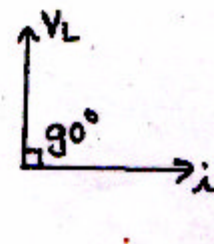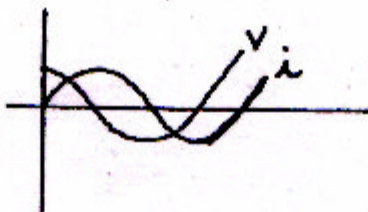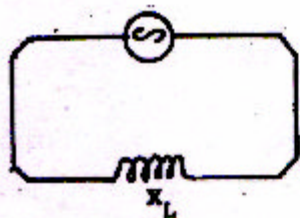

X_L = reaktansi induktif




$$E = L \frac{d i \sin \omega t}{dt}$$

$$E = L \omega i_{\max} \cos \omega t$$

$$X_L = \omega \cdot L$$

(satuan X_L = ohm)

III. Capacitor pada DC-AC

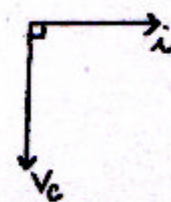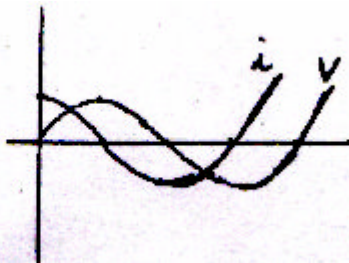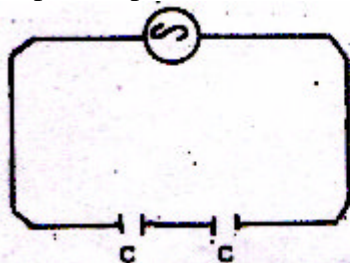

C = kapasitas kapasitor

$$Q = C \cdot V$$

http://www.banksoal.sebarin.com

$X_c =$ reaktansi kapasitif

$$i = \frac{dQ}{dt} = \frac{dc.V}{dt}$$

$$i = \frac{c.dV \max . \sin \omega.t}{dt}$$


$$i = \omega.c.V \max . \cos \omega.t$$

$$X_c = \frac{1}{\omega C}$$

(Satuan $X_c = 0\text{hm}$)

IV. R-L-C dirangkai seri

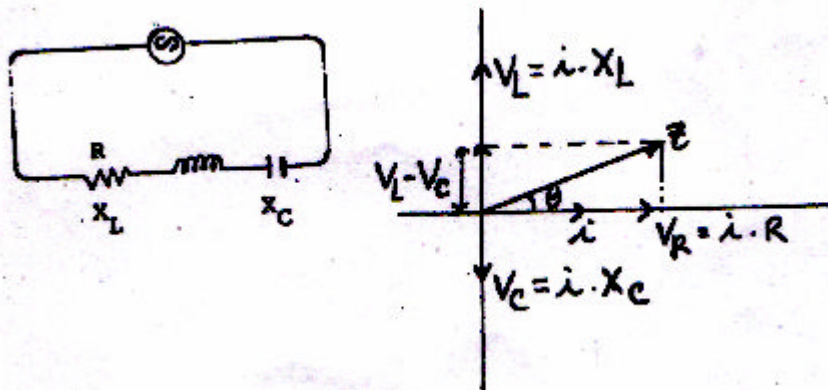1. $X_L = \omega.L$
2. $X_c = \frac{1}{\omega.C}$
3. Gambar fasor



4. $Z = \sqrt{R^2 + (X_L - X_c)^2}$

5. $i = \frac{E}{Z}$

6. $V_{ab} = i.R$ $V_{ac} = \sqrt{V_r^2 + V_l^2}$
 $V_{bc} = i.X_L$ $V_{bd} = V_l - V_c$
 $V_{cd} = i.X_c$ $V_{ad} = \sqrt{V_r^2 + (V_l - V_c)^2}$

7. Daya = $P_{\text{semu}} \cdot \cos \theta$

Daya = $P_{\text{semu}} \cdot \frac{R}{Z}$

$P_{\text{semu}} = V.I$ (Volt Amper)

a. $X_L > X_c \rightarrow$ RLC bersifat induktif

V mendahului I dengan beda fase θ

b. $X_L = X_c \rightarrow$ RLC resonansi

$Z = R \rightarrow$ kuat arus paling besar, karena hambatan total paling kecil.

$$f = \frac{1}{2\pi} \sqrt{\frac{1}{L.C}} \quad T = 2\pi \sqrt{L.C}$$

c. $X_c > X_L \rightarrow$ RLC bersifat kapasitif

I mendahului V dengan beda fase θ

8. $\text{tg } \theta = \frac{X_L - X_C}{R}$

Z = Impedansi

θ = sudut fase

L = induktansi diri

f = frekwensi

T = periode

R = hambatan